

Міністерство освіти і науки України
Національний університет «Львівська політехніка»

Кафедра ЕОМ



Звіт

до лабораторної роботи № 3

з дисципліни «Моделювання комп'ютерних систем»
на тему:

«Поведінковий опис цифрового автомата Перевірка роботи автомата за
допомогою стенда Elbert V2 – Spartan 3A FPGA»

Варіант №15

Виконав:
ст. гр. КІ-201
Коростенська С.В

Прийняв:
ст. викладач
каф. ЕОМ
Козак Н. Б.

Львів 2024

Мета роботи: На базі стенда реалізувати цифровий автомат для обчислення значення виразів.

Виконання роботи:

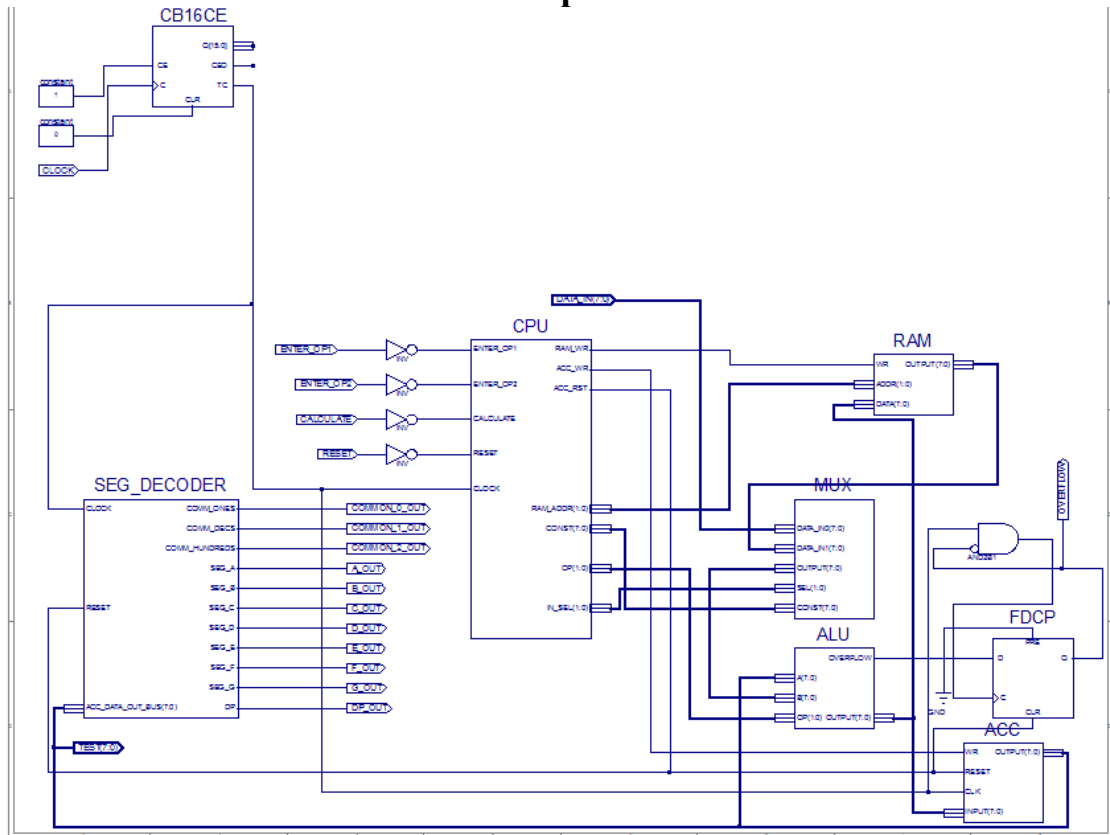


Рис. 1 – Top Level

Файл ACC.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ACC is
    Port ( WR : in STD_LOGIC;
          RESET : in STD_LOGIC;
          CLK : in STD_LOGIC;
          INPUT : in STD_LOGIC_VECTOR (7 downto 0);
          OUTPUT : out STD_LOGIC_VECTOR (7 downto 0));
end ACC;

architecture ACC_arch of ACC is
    signal DATA : STD_LOGIC_VECTOR (7 downto 0);
begin
    process (CLK)

```

```

begin
  if rising_edge(CLK) then
    if RESET = '1' then
      DATA <= (others => '0');
    elsif WR = '1' then
      DATA <= INPUT;
    end if;
  end if;
end process;

OUTPUT <= DATA;

end ACC_arch;

```

```

Файл ALU.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity ALU is
  Port ( A : in  STD_LOGIC_VECTOR(7 downto 0);
        B : in  STD_LOGIC_VECTOR(7 downto 0);
        OP : in  STD_LOGIC_VECTOR(1 downto 0);
        OUTPUT : out STD_LOGIC_VECTOR(7 downto 0);
        OVERFLOW: out STD_LOGIC);
end ALU;

architecture ALU_Behavioral of ALU is
  component FullAdder8 is
    Port ( A: in STD_LOGIC_VECTOR (7 downto 0);
          B: in STD_LOGIC_VECTOR (7 downto 0);
          Ci: in STD_LOGIC;
          S: out STD_LOGIC_VECTOR (7 downto 0);
          Co: out STD_LOGIC);
  end component;
  signal AdderOut: STD_LOGIC_VECTOR(7 downto 0) := (others =>
'0');
  signal Carry: STD_LOGIC;
  signal SEL: STD_LOGIC := '0';
  signal MuxB: STD_LOGIC_VECTOR(7 downto 0) := (others => '0');

```

```

begin
    MuxB <= B when (SEL = '0') else not B;
    Adder: FullAdder8 port map(
        A => A,
        B => MuxB,
        Ci => SEL,
        S => AdderOut,
        Co => Carry
    );
    ALU_EX: process (A, B, OP, Carry, AdderOut)
    begin
        case (OP) is
            when "00" => OUTPUT <= A nor B; OVERFLOW <= '0';
            when "01" => SEL <= '0'; OUTPUT <= AdderOut;
OVERFLOW <= Carry;
            when "10" => SEL <= '1'; OUTPUT <= AdderOut;
OVERFLOW <= not Carry;
            when others => OUTPUT <= B; OVERFLOW <= '1';
        end case;
    end process;
end ALU_Behavioral;

```

```

Файл CPU.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity CPU is
    port( ENTER_OP1 : IN STD_LOGIC;
        ENTER_OP2 : IN STD_LOGIC;
        CALCULATE : IN STD_LOGIC;
        RESET : IN STD_LOGIC;
        CLOCK : IN STD_LOGIC;
        RAM_WR : OUT STD_LOGIC;
        RAM_ADDR : OUT STD_LOGIC_VECTOR(1
DOWNTO 0);
        CONST : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
        ACC_WR : OUT STD_LOGIC;
        ACC_RST : OUT STD_LOGIC;
        IN_SEL : OUT STD_LOGIC_VECTOR(1 downto 0);
        OP : OUT STD_LOGIC_VECTOR(1 DOWNTO 0));
end CPU;

```

architecture CPU_arch of CPU is

```
type STATE_TYPE is (RST, IDLE, LOAD_OP1, LOAD_OP2,
RUN_CALC0, RUN_CALC1, RUN_CALC2, RUN_CALC3, RUN_CALC4,
FINISH);
```

```
signal CUR_STATE : STATE_TYPE;
```

```
signal NEXT_STATE : STATE_TYPE;
```

```
begin
```

```
    SYNC_PROC: process (CLOCK)
```

```
    begin
```

```
        if (rising_edge(CLOCK)) then
```

```
            if (RESET = '1') then
```

```
                CUR_STATE <= RST;
```

```
            else
```

```
                CUR_STATE <= NEXT_STATE;
```

```
            end if;
```

```
        end if;
```

```
    end process;
```

```
    NEXT_STATE_DECODE: process (CLOCK)
```

```
    begin
```

```
        NEXT_STATE <= CUR_STATE;
```

```
        case(CUR_STATE) is
```

```
            when RST =>
```

```
                NEXT_STATE <= IDLE;
```

```
            when IDLE =>
```

```
                if (ENTER_OP1 = '1') then
```

```
                    NEXT_STATE <= LOAD_OP1;
```

```
                elsif (ENTER_OP2 = '1') then
```

```
                    NEXT_STATE <= LOAD_OP2;
```

```
                elsif (CALCULATE = '1') then
```

```
                    NEXT_STATE <= RUN_CALC0;
```

```
                else
```

```
                    NEXT_STATE <= IDLE;
```

```
                end if;
```

```
            when LOAD_OP1 =>
```

```
                NEXT_STATE <= IDLE;
```

```
            when LOAD_OP2 =>
```

```
                NEXT_STATE <= IDLE;
```

```

        when RUN_CALC0 =>
            NEXT_STATE <= RUN_CALC1;
        when RUN_CALC1 =>
            NEXT_STATE <= RUN_CALC2;
        when RUN_CALC2 =>
            NEXT_STATE <= RUN_CALC3;
        when RUN_CALC3 =>
            NEXT_STATE <= RUN_CALC4;
        when RUN_CALC4 =>
            NEXT_STATE <= FINISH;
        when FINISH      =>
            NEXT_STATE <= FINISH;
        when others      =>
            NEXT_STATE <= IDLE;
    end case;
end process;

```

OUTPUT_DECODE: process (CUR_STATE)

begin

case (CUR_STATE) is

when RST =>

```

    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "000000000";
    ACC_WR <= '0';
    ACC_RST <= '1';
    IN_SEL <= "00";
    OP <= "00";

```

when LOAD_OP1 =>

```

    RAM_WR <= '1';
    RAM_ADDR <= "00";
    CONST <= "000000000";
    ACC_WR <= '0';
    ACC_RST <= '1';
    IN_SEL <= "00";
    OP <= "01";

```

when LOAD_OP2 =>

```

    RAM_WR <= '1';
    RAM_ADDR <= "01";
    CONST <= "000000000";
    ACC_WR <= '0';
    ACC_RST <= '1';
    IN_SEL <= "00";

```

```

        OP <= "01";
when RUN_CALC0 =>
    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "00000000";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "01";
    OP <= "01";
when RUN_CALC1 =>
    RAM_WR <= '0';
    RAM_ADDR <= "01";
    CONST <= "00000000";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "01";
    OP <= "00";
when RUN_CALC2 =>
    RAM_WR <= '0';
    RAM_ADDR <= "01";
    CONST <= "00000000";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "01";
    OP <= "01";
when RUN_CALC3 =>
    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "00001010";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "10";
    OP <= "01";
when RUN_CALC4 =>
    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "00000011";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "10";
    OP <= "10";
when IDLE =>
    RAM_WR <= '0';

```

```

        RAM_ADDR <= "00";
        CONST <= "000000000";
        ACC_WR <= '0';
        ACC_RST <= '0';
        IN_SEL <= "00";
        OP <= "01";
    when others =>
        RAM_WR <= '0';
        RAM_ADDR <= "00";
        CONST <= "000000000";
        ACC_WR <= '0';
        ACC_RST <= '0';
        IN_SEL <= "00";
        OP <= "00";
    end case;
end process;
end CPU_arch;

```

Файл FullAdder.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity FullAdder is
    Port (A: in STD_LOGIC;
          B: in STD_LOGIC;
          Ci: in STD_LOGIC;
          S: out STD_LOGIC;
          Co: out STD_LOGIC);
end FullAdder;

architecture Behavioral of FullAdder is
begin
    S <= (A xor B) xor Ci;
    Co <= (A and B) or ((A xor B) and Ci);
end Behavioral;

```

Файл FullAdder8.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity FullAdder8 is
    Port ( A: in STD_LOGIC_VECTOR (7 downto 0);
          B: in STD_LOGIC_VECTOR (7 downto 0);

```



```

        Ci: in STD_LOGIC;
        S: out STD_LOGIC_VECTOR (7 downto 0);
        Co: out STD_LOGIC);
end FullAdder8;

architecture Behavioral of FullAdder8 is
    component FullAdder is
        Port (A: in STD_LOGIC;
              B: in STD_LOGIC;
              Ci: in STD_LOGIC;
              S: out STD_LOGIC;
              Co: out STD_LOGIC);
    end component;
    signal carry: STD_LOGIC_VECTOR(8 downto 0) := (others =>
'0');
begin
    carry(0) <= Ci;
    FullAdderGenerate: for i in 0 to 7 generate
    adder: FullAdder port map(
        A => A(i),
        B => B(i),
        Ci => carry(i),
        S => S(i),
        Co => carry(i + 1)
    );
    end generate FullAdderGenerate;
    Co <= carry(8);
end Behavioral;

```

Файл MUX.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity MUX is
```

```
    PORT(
```

```
        SEL: in STD_LOGIC_VECTOR(1 downto 0);
```

```
        CONST: in STD_LOGIC_VECTOR(7 downto 0);
```

```
        --CONST1: in STD_LOGIC_VECTOR()
```

```
        DATA_IN0: in STD_LOGIC_VECTOR(7 downto 0);
```

```
        DATA_IN1: in STD_LOGIC_VECTOR(7 downto 0);
```

```
        OUTPUT: out STD_LOGIC_VECTOR(7 downto 0)
```

```
    );
```

```

end MUX;

architecture Behavioral of MUX is
begin
    process (SEL, DATA_IN0, DATA_IN1, CONST)
    begin
        if (SEL = "00") then
            OUTPUT <= DATA_IN0;
        elsif (SEL = "01") then
            OUTPUT <= DATA_IN1;
        else
            OUTPUT <= CONST;
        end if;
    end process;
end Behavioral;

```

```

Файл RAM.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity RAM is
    port(
        WR : IN STD_LOGIC;
        ADDR : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
        DATA : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
        OUTPUT : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
    );
end RAM;

architecture RAM_arch of RAM is
    type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR(7
downto 0);
    signal UNIT : ram_type;
begin
    process(ADDR, UNIT, WR, DATA)
    begin
        if (WR = '1') then
            UNIT(conv_integer(ADDR)) <= DATA;

```

```
        end if;  
        OUTPUT <= UNIT(conv_integer(ADDR));  
    end process;
```

```
end RAM_arch;
```

Файл SEG_DECODER.vhd

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
entity SEG_DECODER is  
    port( CLOCK : IN STD_LOGIC;  
          RESET : IN STD_LOGIC;  
          ACC_DATA_OUT_BUS : IN STD_LOGIC_VECTOR(7  
DOWNTO 0);  
          COMM_ONES          : OUT STD_LOGIC;  
          COMM_DECS          : OUT STD_LOGIC;  
          COMM_HUNDREDS      : OUT STD_LOGIC;  
          SEG_A              : OUT STD_LOGIC;  
          SEG_B              : OUT STD_LOGIC;  
          SEG_C              : OUT STD_LOGIC;  
          SEG_D              : OUT STD_LOGIC;  
          SEG_E              : OUT STD_LOGIC;  
          SEG_F              : OUT STD_LOGIC;  
          SEG_G              : OUT STD_LOGIC;  
          DP                 : OUT STD_LOGIC);  
end SEG_DECODER;  
  
architecture Behavioral of SEG_DECODER is  
  
    signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";  
    signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0001";  
    signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) :=  
"0000";  
  
begin  
    BIN_TO_BCD : process (ACC_DATA_OUT_BUS)  
        variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;
```

```

variable bcd    : STD_LOGIC_VECTOR(11 downto 0);
begin
  bcd          := (others => '0');
  hex_src      := ACC_DATA_OUT_BUS;

  for i in hex_src'range loop
    if bcd(3 downto 0) > "0100" then
      bcd(3 downto 0) := bcd(3 downto 0) + "0011" ;
    end if ;
    if bcd(7 downto 4) > "0100" then
      bcd(7 downto 4) := bcd(7 downto 4) + "0011" ;
    end if ;
    if bcd(11 downto 8) > "0100" then
      bcd(11 downto 8) := bcd(11 downto 8) + "0011" ;
    end if ;

    bcd := bcd(10 downto 0) & hex_src(hex_src'left) ; -- shift bcd + 1 new
entry
    hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ; --
shift src + pad with 0
  end loop ;

  HONDREDS_BUS    <= bcd (11 downto 8);
  DECS_BUS        <= bcd (7 downto 4);
  ONES_BUS         <= bcd (3 downto 0);

end process BIN_TO_BCD;

INDICATE : process(CLOCK)
  type DIGIT_TYPE is (ONES, DECS, HUNDREDS);

  variable CUR_DIGIT    : DIGIT_TYPE := ONES;
  variable DIGIT_VAL     : STD_LOGIC_VECTOR(3 downto 0)
:= "0000";
  variable DIGIT_CTRL    : STD_LOGIC_VECTOR(6 downto 0)
:= "00000000";
  variable COMMONS_CTRL : STD_LOGIC_VECTOR(2
downto 0) := "000";

  begin
    if (rising_edge(CLOCK)) then
      if(RESET = '0') then
        case CUR_DIGIT is

```

```

when ONES =>
    DIGIT_VAL := ONES_BUS;
    CUR_DIGIT := DECS;
    COMMONS_CTRL := "001";
when DECS =>
    DIGIT_VAL := DECS_BUS;
    CUR_DIGIT := HUNDREDS;
    COMMONS_CTRL := "010";
when HUNDREDS =>
    DIGIT_VAL :=
HONDREDS_BUS;

    CUR_DIGIT := ONES;
    COMMONS_CTRL := "100";
when others =>
    DIGIT_VAL := ONES_BUS;
    CUR_DIGIT := ONES;
    COMMONS_CTRL := "000";
end case;

case DIGIT_VAL is      --abcdefg
    when "0000" => DIGIT_CTRL :=
"1111110";
    when "0001" => DIGIT_CTRL :=
"0110000";
    when "0010" => DIGIT_CTRL :=
"1101101";
    when "0011" => DIGIT_CTRL :=
"1111001";
    when "0100" => DIGIT_CTRL :=
"0110011";
    when "0101" => DIGIT_CTRL :=
"1011011";
    when "0110" => DIGIT_CTRL :=
"1011111";
    when "0111" => DIGIT_CTRL :=
"1110000";
    when "1000" => DIGIT_CTRL :=
"1111111";
    when "1001" => DIGIT_CTRL :=
"1111011";
    when others => DIGIT_CTRL :=
"0000000";
end case;

```

```

else
    DIGIT_VAL := ONES_BUS;
    CUR_DIGIT := ONES;
    COMMONS_CTRL := "000";
end if;

COMM_ONES    <= not COMMONS_CTRL(0);
COMM_DECS    <= not COMMONS_CTRL(1);
COMM_HUNDREDS <= not
COMMONS_CTRL(2);

SEG_A <= not DIGIT_CTRL(6);
SEG_B <= not DIGIT_CTRL(5);
SEG_C <= not DIGIT_CTRL(4);
SEG_D <= not DIGIT_CTRL(3);
SEG_E <= not DIGIT_CTRL(2);
SEG_F <= not DIGIT_CTRL(1);
SEG_G <= not DIGIT_CTRL(0);
DP    <= '1';

end if;
end process INDICATE;

end Behavioral;

```

 


Рис. 2 – Часова діаграма ACC

 


Рис. 3 – Часова діаграма ALU

 


Рис. 4 – Часова діаграма MUX

 


Рис. 5 – Часова діаграма RAM



Рис 6. – Часова діаграма SEG_DECODER

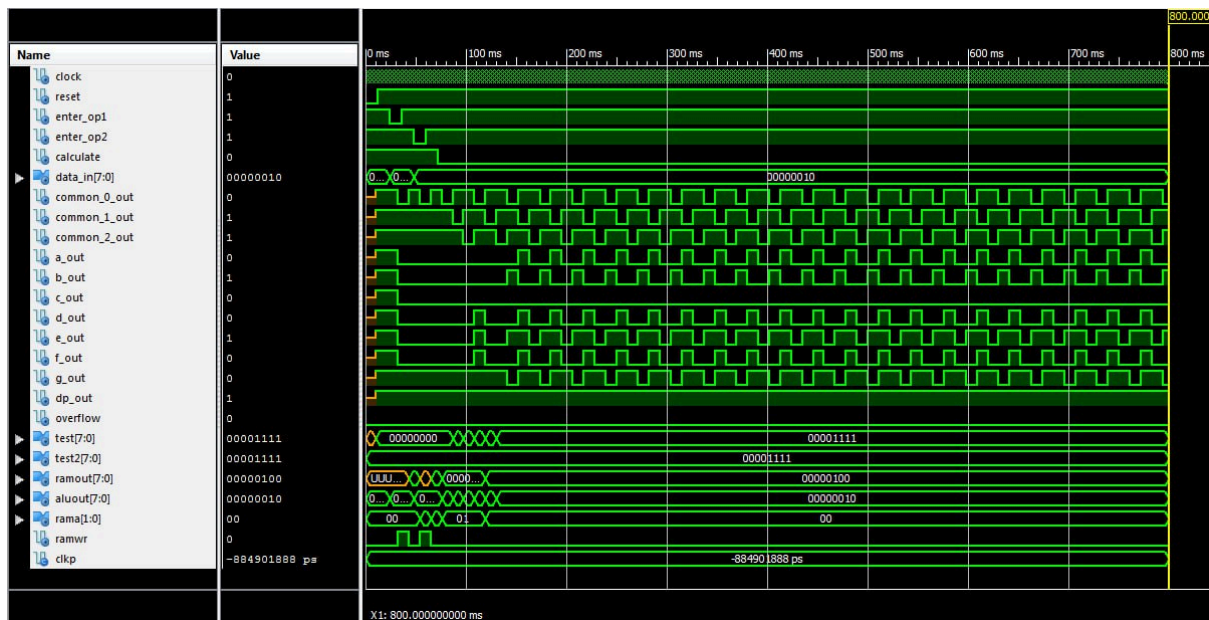


Рис 7. – Часова діаграма TopLevel

```

Файл TopLevelTest.vhd
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
LIBRARY UNISIM;
USE UNISIM.Vcomponents.ALL;
ENTITY TopLevel_TopLevel_sch_tb IS
END TopLevel_TopLevel_sch_tb;
ARCHITECTURE behavioral OF TopLevel_TopLevel_sch_tb IS

    COMPONENT TopLevel
    PORT( CLOCK :      IN   STD_LOGIC;

```



```

RESET      :      IN      STD_LOGIC;
ENTER_OP1   :      IN      STD_LOGIC;
ENTER_OP2   :      IN      STD_LOGIC;
CALCULATE   :      IN      STD_LOGIC;
DATA_IN     :      IN      STD_LOGIC_VECTOR (7 DOWNT0 0);
COMMON_0_OUT :      OUT STD_LOGIC;
COMMON_1_OUT :      OUT STD_LOGIC;
COMMON_2_OUT :      OUT STD_LOGIC;
            TEST: OUT STD_LOGIC_VECTOR(7 downto 0);
A_OUT       :      OUT STD_LOGIC;
B_OUT       :      OUT STD_LOGIC;
C_OUT       :      OUT STD_LOGIC;
D_OUT       :      OUT STD_LOGIC;
E_OUT       :      OUT STD_LOGIC;
F_OUT       :      OUT STD_LOGIC;
G_OUT       :      OUT STD_LOGIC;
DP_OUT      :      OUT STD_LOGIC;
OVERFLOW    :      OUT STD_LOGIC);
END COMPONENT;

```

```

SIGNAL CLOCK      :      STD_LOGIC := '0';
SIGNAL RESET :      STD_LOGIC;
SIGNAL ENTER_OP1 :      STD_LOGIC;
SIGNAL ENTER_OP2 :      STD_LOGIC;
SIGNAL CALCULATE :      STD_LOGIC;
SIGNAL DATA_IN   :      STD_LOGIC_VECTOR (7 DOWNT0 0);
SIGNAL COMMON_0_OUT :      STD_LOGIC;
SIGNAL COMMON_1_OUT :      STD_LOGIC;
SIGNAL COMMON_2_OUT :      STD_LOGIC;
SIGNAL A_OUT:      STD_LOGIC;
SIGNAL B_OUT:      STD_LOGIC;
SIGNAL C_OUT:      STD_LOGIC;
SIGNAL D_OUT      :      STD_LOGIC;
SIGNAL E_OUT:      STD_LOGIC;
SIGNAL F_OUT:      STD_LOGIC;
SIGNAL G_OUT      :      STD_LOGIC;
SIGNAL DP_OUT      :      STD_LOGIC;
SIGNAL OVERFLOW :      STD_LOGIC;
SIGNAL TEST: STD_LOGIC_VECTOR(7 downto 0);
SIGNAL TEST1: STD_LOGIC_VECTOR(7 downto 0);
SIGNAL TEST2: STD_LOGIC_VECTOR(7 downto 0);

```

```
-- constant CLOCK_period : time := 166ns;
```

```
constant CLKP: time := 24ms;--48ms;
```

```
BEGIN
```

```
UUT: TopLevel PORT MAP(  
    CLOCK => CLOCK,  
    RESET => RESET,  
    ENTER_OP1 => ENTER_OP1,  
    ENTER_OP2 => ENTER_OP2,  
    CALCULATE => CALCULATE,  
    DATA_IN => DATA_IN,  
    COMMON_0_OUT => COMMON_0_OUT,  
    COMMON_1_OUT => COMMON_1_OUT,  
    COMMON_2_OUT => COMMON_2_OUT,  
    A_OUT => A_OUT,  
    B_OUT => B_OUT,  
    C_OUT => C_OUT,  
    D_OUT => D_OUT,  
    E_OUT => E_OUT,  
    F_OUT => F_OUT,  
    G_OUT => G_OUT,  
    DP_OUT => DP_OUT,  
    OVERFLOW => OVERFLOW,  
    TEST => TEST  
);
```

```
    CLOCK_process: process  
begin  
    CLOCK <= '0';  
    wait for 83ns;  
    CLOCK <= '1';  
    wait for 83ns;  
end process;
```

```
-- *** Test Bench - User Defined Section ***
```

```
tb : PROCESS
```

```
BEGIN
```

```
--ENTER_OP1 <= '0';  
--ENTER_OP2 <= '0';  
--CALCULATE <= '0';  
--DATA_IN <= (others => '0');  
--RESET <= '1';  
--wait for CLKP * 4;
```

```

--RESET <= '0';
--DATA_IN <= "00000000"; -- A
--ENTER_OP1 <= '1';
--wait for CLKP * 4;
--ENTER_OP1 <= '0';
--wait for CLKP * 4;
--DATA_IN <= "00000001"; -- B
--ENTER_OP2 <= '1';
--wait for CLKP * 4;
--ENTER_OP2 <= '0';
--wait for CLKP * 4;
--CALCULATE <= '1'; -- START CALCULATION

```

```

lp1: for i in 1 to 1 loop
    lp2: for j in 2 to 2 loop
        TEST1 <= std_logic_vector(to_unsigned(i, 8)) nor
std_logic_vector(to_unsigned(j, 8));
        TEST2 <=
std_logic_vector(to_unsigned(to_integer(signed(std_logic_vector(to_signed(i,
8)) nor std_logic_vector(to_unsigned(j, 8)))) + j + 7, 8));
        ENTER_OP1 <= '1';
        ENTER_OP2 <= '1';
        CALCULATE <= '1';
        DATA_IN <= (others => '0');
        RESET <= '0';
        wait for CLKP;
        RESET <= '1';
        wait for CLKP;
        DATA_IN <= std_logic_vector(to_unsigned(i, 8)); --
A
        ENTER_OP1 <= '0';
        wait for CLKP;
        ENTER_OP1 <= '1';
        wait for CLKP;
        DATA_IN <= std_logic_vector(to_unsigned(j, 8)); --
B
        ENTER_OP2 <= '0';
        wait for CLKP;
        ENTER_OP2 <= '1';
        wait for CLKP;
        CALCULATE <= '0'; -- START CALCULATION
        wait for CLKP* 7;
        assert TEST = TEST2 severity FAILURE;

```

```

        wait for CLKP;
    end loop;
end loop;

WAIT; -- will wait forever
END PROCESS;
-- *** End Test Bench - User Defined Section ***

END;
```

 


Рис.8 – 7-сегментний індикатор

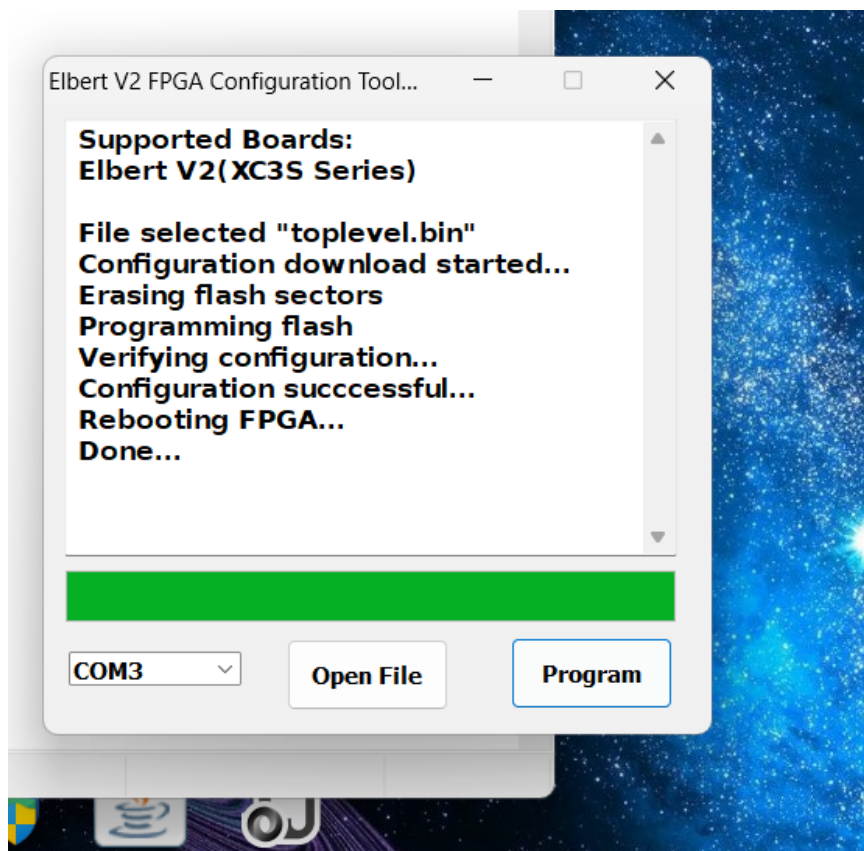


Рис.9 – Успішна прошивка

Висновок: Виконуючи дану лабораторну роботу я навчилася реалізовувати цифровий автомат для обчислення значення виразів використовуючи засоби VHDL.